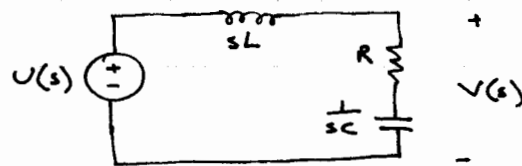


Problem Set 1

1) Transforming the circuit using Laplace transforms:



Voltage divider gives:

$$V(s) = \frac{R + \frac{1}{sC}}{R + \frac{1}{sC} + sL} \times U(s)$$

$$= \frac{RCs + 1}{RCs + 1 + LCs^2} \times U(s)$$

$$\Rightarrow (LCs^2 + RCs + 1) V(s) = (RCs + 1) U(s)$$

$$\Rightarrow (s^2 + \frac{R}{L}s + \frac{1}{LC}) V(s) = (\frac{R}{L}s + \frac{1}{LC}) U(s)$$

Taking inverse Laplace transforms,

$$\frac{d^2 u}{dt^2} + \frac{R}{L} \frac{du}{dt} + \frac{1}{LC} u(t) = \frac{R}{L} \frac{du}{dt} + \frac{1}{LC} u(t)$$

2) KCL gives

$$-u(t) + u_L + u_R + u_C = 0$$

$$\Rightarrow L \frac{di_L}{dt} + R i_L + u_C = u(t)$$

Also,

$$i_L = C \frac{du_C}{dt}$$

and

$$u(t) = u_R + u_C$$

$$= R i_L + u_C$$

Writing in state space form

$$\begin{bmatrix} \dot{u}_C \\ \dot{i}_L \end{bmatrix} = \begin{bmatrix} 0 & \frac{1}{C} \\ -\frac{1}{L} & -\frac{R}{L} \end{bmatrix} \begin{bmatrix} u_C \\ i_L \end{bmatrix} + \begin{bmatrix} 0 \\ \frac{1}{L} \end{bmatrix} u(t)$$

$$u(t) = \begin{bmatrix} 1 & R \end{bmatrix} \begin{bmatrix} u_C \\ i_L \end{bmatrix}$$

3) ... The controllable canonical realization is given directly from ... the differential equation as,

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -\frac{1}{LC} & -\frac{R}{L} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ 1 \end{bmatrix} u(t)$$

$$u(t) = \begin{bmatrix} \frac{1}{LC} & \frac{R}{L} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}$$

4) ... Comparing the output equations for the two state space forms, ... it appears that,

$$u_c = \frac{1}{LC} x_1, \quad i_L = \frac{1}{L} x_2$$

Substituting these equivalences into the state space form of part (2),

$$\frac{1}{LC} \dot{x}_1 = \frac{1}{L} \times \left(\frac{1}{L} x_2 \right) \Rightarrow \dot{x}_1 = x_2$$

$$\frac{1}{L} \dot{x}_2 = -\frac{1}{L} \times \left(\frac{1}{LC} x_1 \right) - \frac{R}{L} \times \left(\frac{1}{L} x_2 \right) + \frac{1}{L} u(t)$$

$$\Rightarrow \dot{x}_2 = -\frac{1}{LC} x_1 - \frac{R}{L} x_2 + u(t)$$

The equations for \dot{x}_1 and \dot{x}_2 can be rewritten,

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -\frac{1}{LC} & -\frac{R}{L} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ 1 \end{bmatrix} u(t)$$

...which exactly matches the form of part (3).

(Note: In general the transformation between realizations is not so simple.)

5) ... The circuit is a series RLC circuit, so overdamped behaviour ... corresponds to


$$\alpha > \omega_0 \Rightarrow \frac{R}{2L} > \frac{1}{\sqrt{LC}}$$

$$\Rightarrow R > \frac{2L}{\sqrt{LC}} = \frac{2}{\sqrt{2}} = \sqrt{2}$$

The plot corresponds to $R = 2 \Omega$ (overdamped)

6) ... $R = 0.5 \Omega$ (underdamped)

Overdamped response

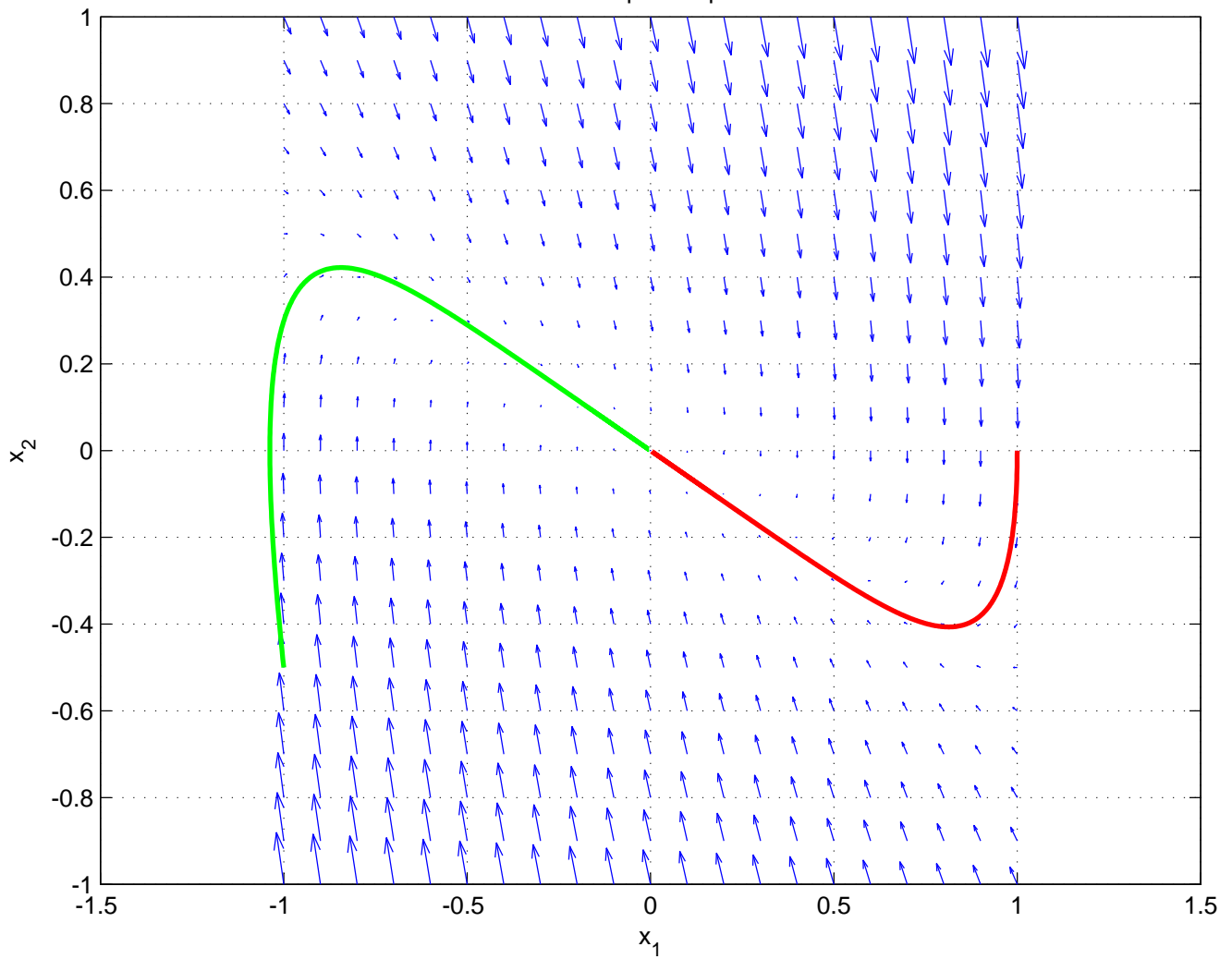

Underdamped response

