

ECE 376 Homework 3 Solutions

H3.1

CONSISTENT UNITS V-MA-K-mW

6.14

$$\frac{V_{out}^2}{10k} = 150mW$$

$$V_{out} = \sqrt{1500} = \boxed{38.73V}$$



NON-INVERTING AMP: $V_{out} = (1 + \frac{1k}{R})5$

$$\frac{38.73}{5} - 1 = \frac{1}{R}$$


$$R = \boxed{.1482k}$$

6.26 SIMPLIFICATIONS

① $4.7M || (1k + 300\Omega) = 4700 || 1.3 = \boxed{1.3k}$
TO 3 SIG FIGS

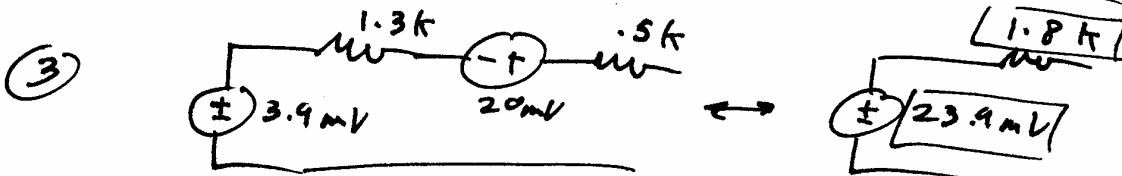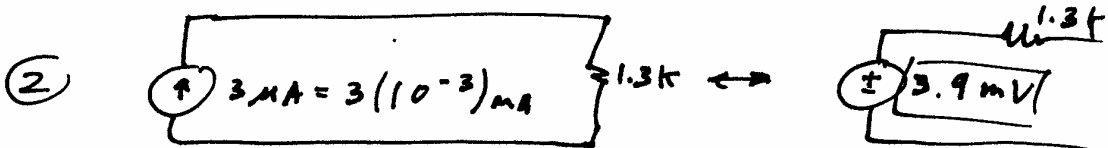

④ $33k + 4.7k = \boxed{37.7k}$

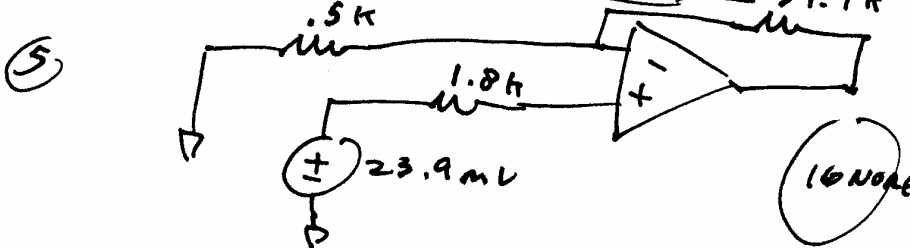


NON-INVERTING

$$V_{out} = (1 + \frac{37.7}{.9}) 23.9mV = \boxed{1.826V}$$

6.28 SOURCE TRANSFORM

2 INVERTING AMPS

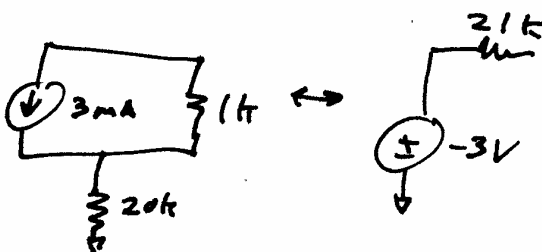

$$V_x = -\frac{100}{21}(-3) - \left(-\frac{100}{10}\right)5 = \boxed{64.29V}$$

6.37


$$v_{out} = (1V) \left(-\frac{20}{2} \right) \left(-\frac{1}{10} \right) = \boxed{1V}$$

1ST INVERTING
STAGE

H 3.2

2ND INVERTING
STAGE

6.40

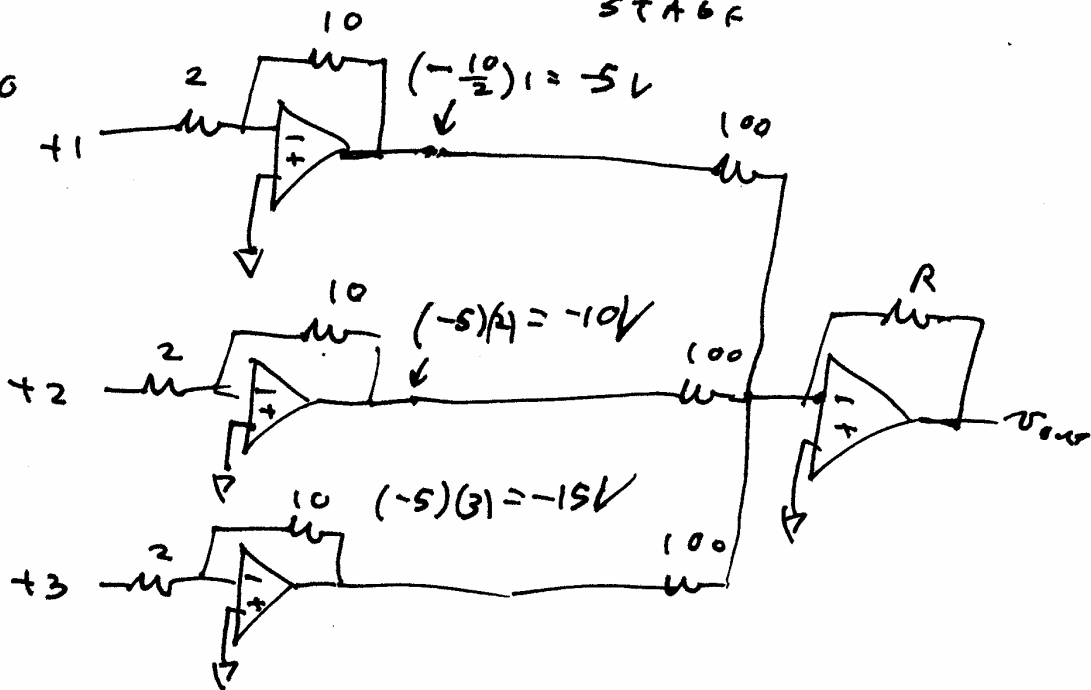

$$\text{SUPERPOSITION } v_{out} = \frac{-R}{100}(-5) + \frac{-R}{100}(-10) + \frac{-R}{100}(-15)$$

$$v_{out} = R(5 + 10 + 15)/100 = R \frac{30}{100} = 10V$$

$$R = \frac{100 \cdot 10}{30} = \frac{1000}{30} = \boxed{33.3 \Omega}$$