

COSINES, SINES, COMPLEX NUMBERS,
AC CIRCUITS IN A NUTSHELL

AC VOLTAGE AND CURRENT

$$v_1(t) = 20 \cos 50t$$

$$v_2(t) = 12 \cos 40t + 30^\circ$$


$$v_3(t) = 8 \cos 2\pi 60t - 90^\circ$$

$$= 8 \sin 2\pi 60t$$

PHASOR - REPRESENT COSINE WAVE
AS COMPLEX NUMBER

$$V = |V| \angle \theta_v = |V| e^{j\theta_v} \quad \text{POLAR}$$


$$= |V| \cos \theta_v + j |V| \sin \theta_v$$

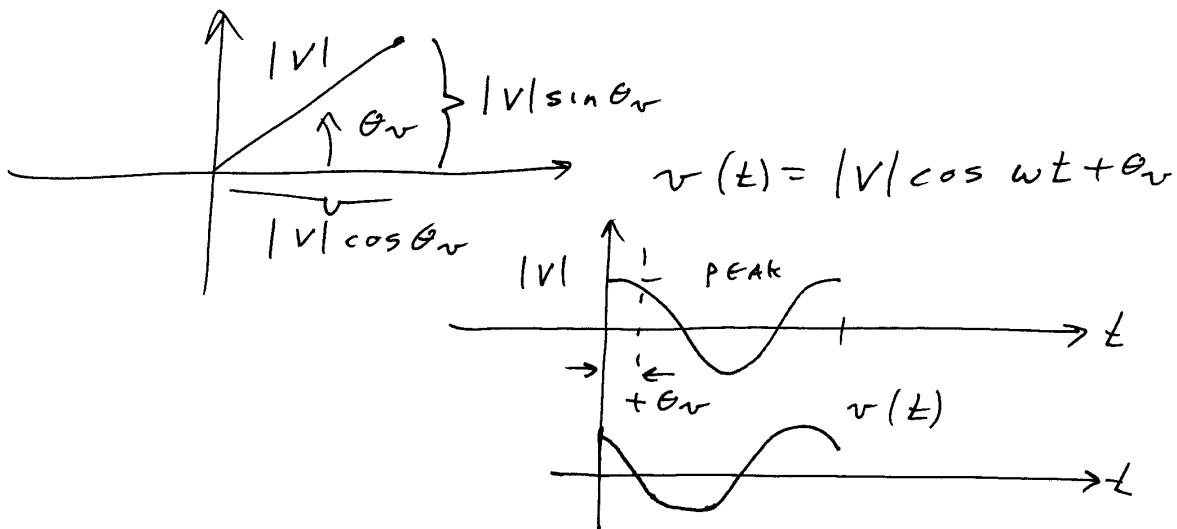


WHEN DO WE MULTIPLY PHASORS?

WHEN WE DO


$$v(t) = R i(t)$$

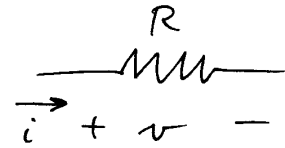

$$v(t) = L \frac{di(t)}{dt}$$

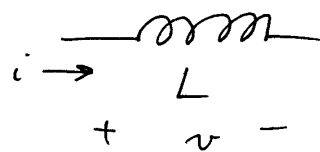

$$v(t) = \frac{1}{C} \int i(t) dt$$

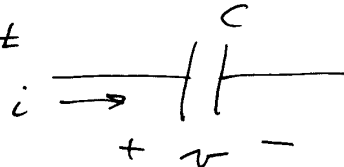

RESISTOR WAVEFORM

$$v(t) = R i(t)$$

FOR $i(t) = \cos \omega t$

$$v(t) = R \cos \omega t$$

PHASOR

$$V = R I$$

$$= R \cdot 1 \angle 0^\circ$$

$$= R \angle 0^\circ$$

INDUCTOR

$$v(t) = L \frac{di(t)}{dt}$$

$$= -\omega L \sin \omega t$$

$$= \omega L \cos \omega t + 90^\circ$$

$$V = j\omega L I$$

$$= \omega L \angle 90^\circ | \angle 0^\circ$$

$$= \omega L \angle 90^\circ$$

CAPACITOR

$$v(t) = \frac{1}{C} \int i(t) dt$$

$$= \frac{1}{\omega C} \sin \omega t$$

$$= \frac{1}{\omega C} \cos \omega t - 90^\circ$$

$$V = \frac{1}{j\omega C} I$$


$$= \left(\frac{-j}{\omega C} \right) (1)$$

$$= \frac{1}{\omega C} \angle -90^\circ | \angle 0^\circ$$

$$= \frac{1}{\omega C} \angle -90^\circ$$

WHEN DO WE ADD PHASORS?

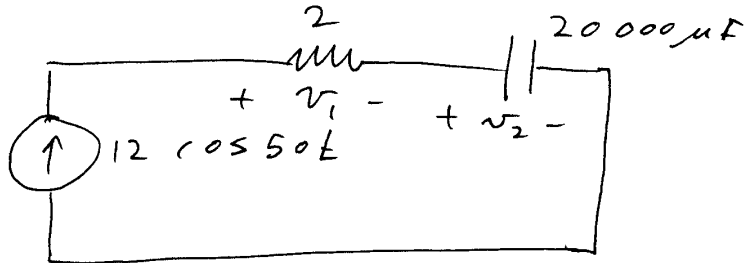WHEN WE DO KVL, KCL TO
ADD VOLTAGE OR CURRENT WAVEFORMS



$$V_1 = 2 I_S = (2)(12) = 24 \angle 0^\circ$$

$$v_1(t) = 24 \cos 50t$$

$$V_2 = \frac{1}{j\omega C} I_S = \frac{1}{j 50 (20000) 10^{-6}} I_S$$

$$= (1 \angle -90^\circ)(12) = 12 \angle -90^\circ$$

$$v_2(t) = 12 \cos 50t - 90^\circ = 12 \sin 50t$$

LISTEN TO ME NOW

BELIEVE ME LATER


$$v_2(t) = \frac{1}{C} \int 12 \cos 50t dt$$

$$= \frac{1}{50C} 12 \sin 50t$$

$$= \frac{1}{50 (20000) 10^{-6}} 12 \sin 50t$$

$$= 12 \sin 50t$$

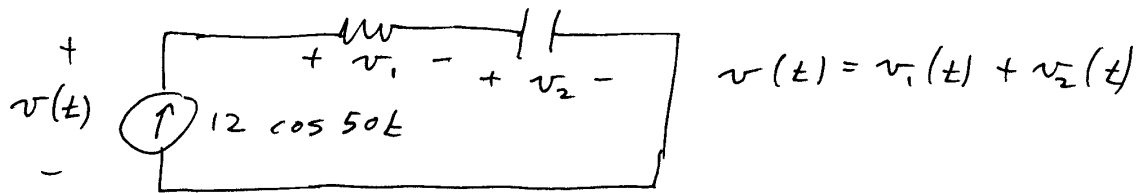BUT PROFESSOR, HOW DO WE
ADD PHASORS (AND WAVEFORMS)?



$$v(t) = 24 \cos 50t + 12 \sin 50t = ?$$

$$V = 24 \angle 0^\circ + 12 \angle -90^\circ = ?$$

$$= 24 + j0 + 0 - j12$$


$$= 24 - j12$$

$$v(t) = 24 \cos 50t + 12 \sin 50t \quad \text{NO GAIN}$$

$$V = 26.8 \angle -26.6^\circ$$

$$v(t) = 26.8 \cos 50t - 26.6^\circ$$

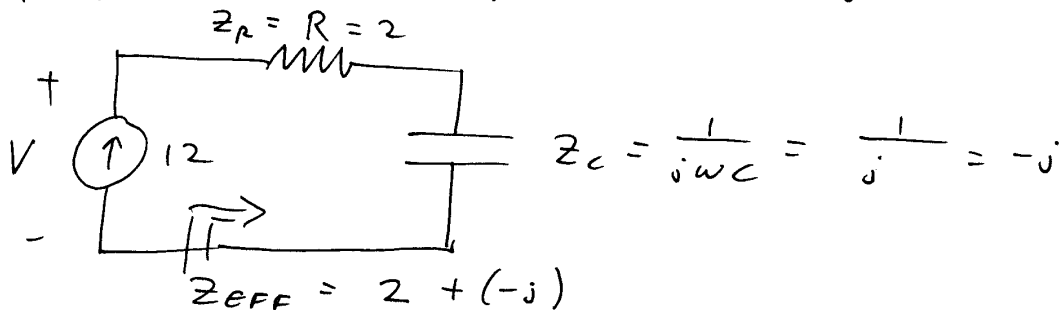IMPEDANCE $Z_R = R$ $Z_C = \frac{1}{j\omega C}$ $Z_L = j\omega L$




$$V = (Z_{EFF})(I) = (2 - j)(12)$$

$$= 24 - j12 = 26.8 \angle -26.6^\circ$$

$$v(t) = 26.8 \cos 50t - 26.6^\circ$$


How ABOUT

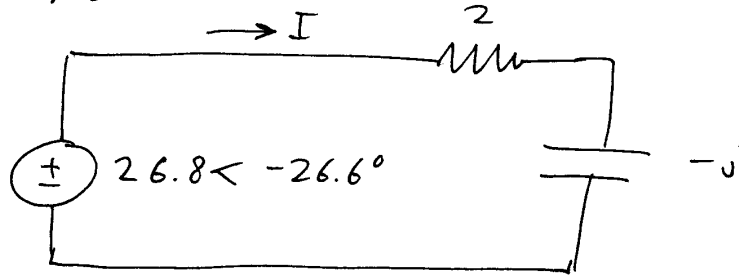

$$I = \frac{V}{Z_{\text{EFF}}} = \frac{V}{2 - j}$$
$$= \frac{26.8 \angle -26.6^\circ}{2.236 \angle -26.6^\circ} = 12 \angle 0^\circ$$

$$i(t) = 12 \cos 50t$$

How ABOUT

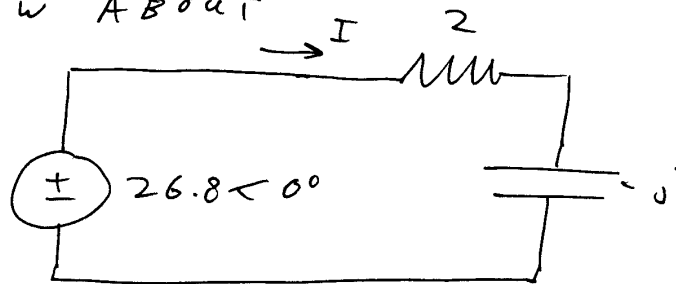

$$I = \frac{26.8 \angle 0^\circ}{2 - j} = \frac{26.8 \angle 0^\circ}{2.236 \angle -26.6^\circ}$$
$$= 12 \angle +26.6^\circ$$

$$i(t) = 12 \cos 50t + 26.6^\circ$$

WHAT IF $V = 53.6 \angle 0^\circ$?

$$i(t) = \underline{\hspace{2cm}}$$