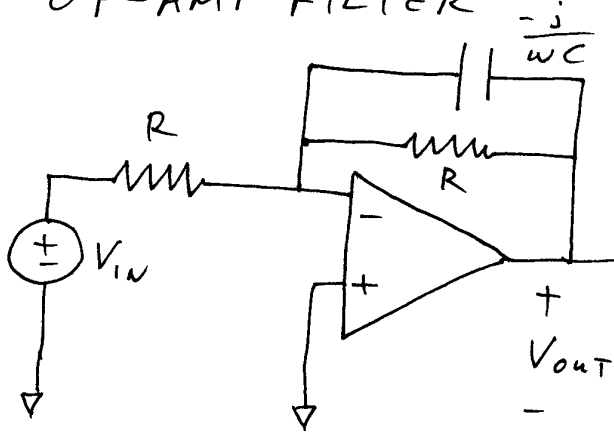


OP-AMP FILTER



$$V_{out} = \frac{-Z_F}{Z_i} V_{IN}$$


$$Z_F = R \parallel \frac{-j}{\omega C}$$

$$= \frac{(R) \left(\frac{-j}{\omega C} \right)}{R - \frac{j}{\omega C}}$$

$$V_{out} = H V_{IN} \quad -H = \frac{+Z_F}{Z_{IN}} = \frac{\frac{-j}{\omega C}}{R - \frac{j}{\omega C}} = \frac{1}{1 + j\omega RC}$$

$$-H = \frac{1}{1 + j\frac{\omega}{\omega_c}} \quad \omega_c = \frac{1}{RC}$$

NON OP-AMP FILTER

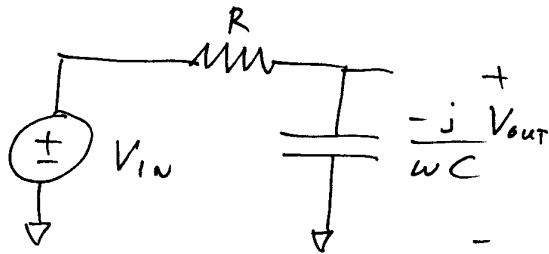

PHASOR VOLTAGE
DIVIDER

$$H = \frac{\frac{-j}{\omega C}}{R - \frac{j}{\omega C}} = \frac{1}{1 + j\omega RC}$$

FOR BOTH FILTERS

$$|H| = \frac{1}{\sqrt{1 + \frac{\omega^2}{\omega_c^2}}} = \frac{1}{\sqrt{2}} \quad \text{WHEN } \omega = \omega_c$$


$$\approx 1 \quad \text{WHEN } \omega = .1\omega_c$$

$$\approx .1 \quad \text{WHEN } \omega = 10\omega_c$$

$$\angle H = -\tan^{-1} \frac{\omega}{\omega_c} = -45^\circ \quad \omega = \omega_c$$

$$\approx 0^\circ \quad \omega = .1\omega_c$$
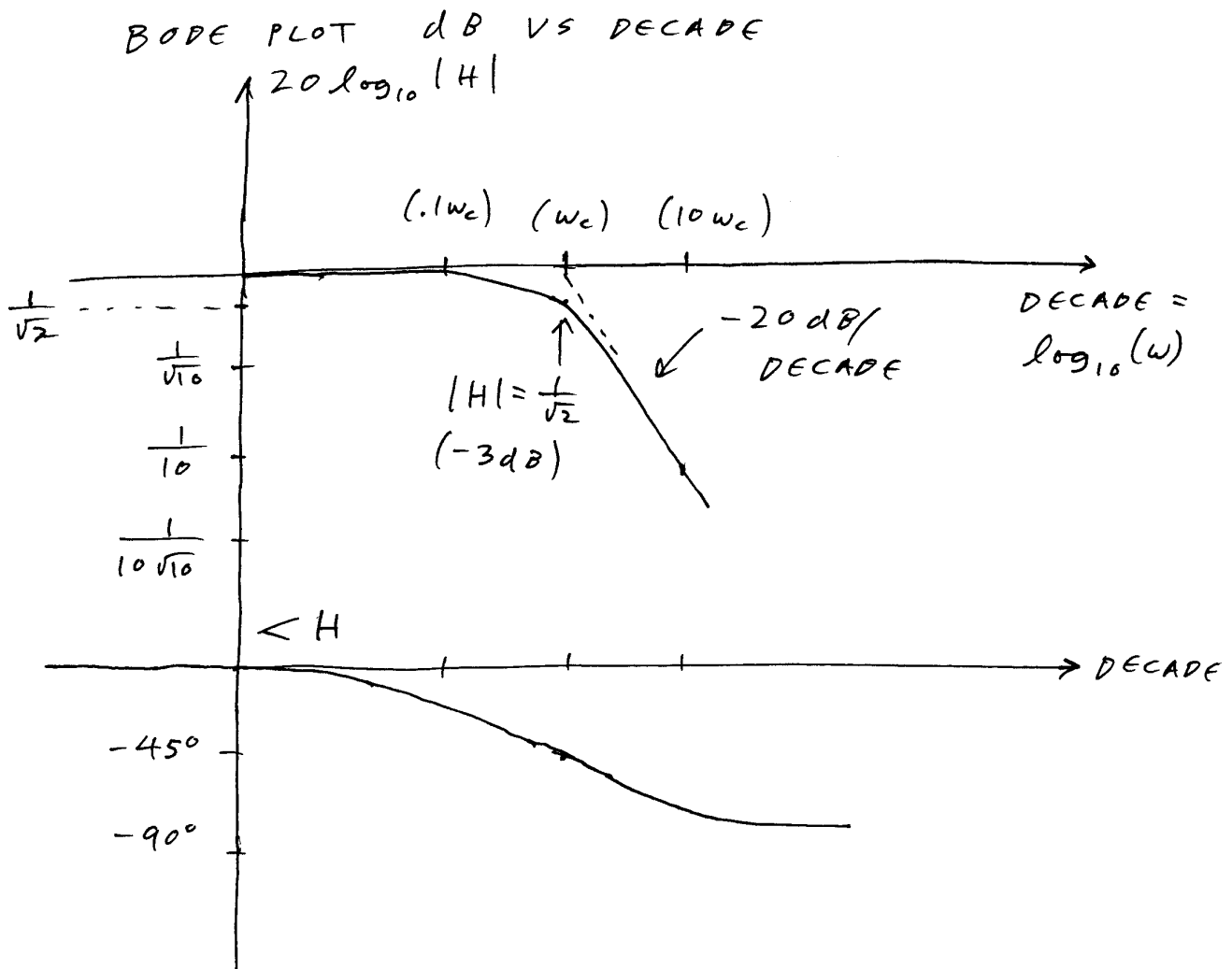
$$\approx -90^\circ \quad \omega = 10\omega_c$$



$$\text{LET } R = 1000 \Omega$$

DESIGN FOR

$$|H| = .9 \quad \text{AT } \omega = 2000 \quad \omega_c = ?$$

$$C = ?$$

$$\frac{1}{\sqrt{1 + \frac{2000^2}{\omega_c^2}}} = .9$$

$$1 + \frac{2000^2}{\omega_c^2} = \frac{1}{(.9)^2}$$

$$(2000)^2 = \omega_c^2 \left(\frac{1}{(.9)^2} - 1 \right) \quad \omega_c = 4129$$

$$\frac{1}{RC} = \omega_c \quad C = \frac{1}{R \omega_c} = \frac{1}{(1000)(4129)}$$
$$= .242 \mu\text{F}$$

DESIGN FOR $\angle H = -15^\circ$ AT $\omega = 400$


MUST BE LEGAL $\omega_c = ?$
 $0 \leq \angle H \leq -90^\circ$ $C = ?$

$$-15^\circ = -\tan^{-1} \frac{\omega}{\omega_c}$$

$$\omega = \omega_c \tan 15^\circ$$


$$\omega_c = \frac{\omega}{\tan 15^\circ} = 1492$$
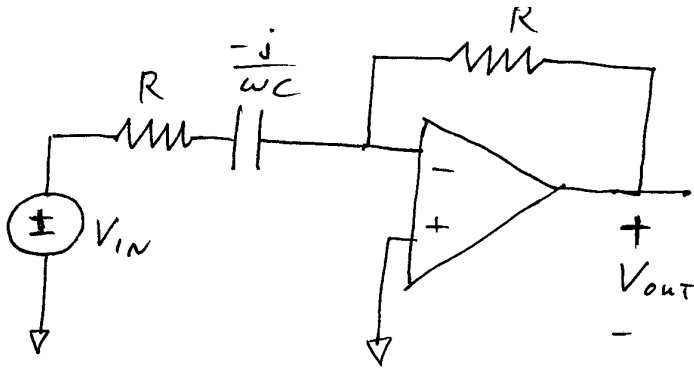
$$C = \frac{1}{R \omega_c} = \frac{1}{(1000)(1492)} = .67 \mu\text{F}$$



$$\begin{aligned}
 -H &= -\frac{V_{out}}{V_{in}} = \frac{Z_F}{Z_I} = \frac{R}{R - \frac{j}{\omega C}} \\
 &= \frac{1}{1 + \frac{\omega C}{j\omega}} \qquad \omega_c = \frac{1}{RC}
 \end{aligned}$$

NON OP-AMP VERSION

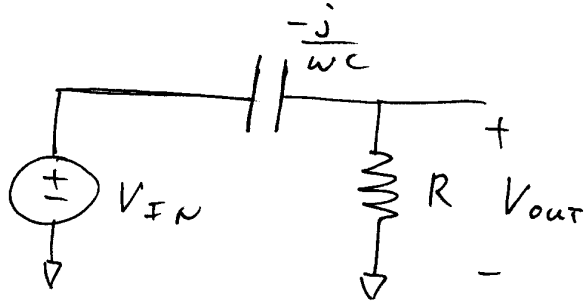

$$\begin{aligned}
 H &= \frac{R}{R - \frac{j}{\omega C}} \\
 &= \frac{1}{1 + \frac{\omega C}{j\omega}}
 \end{aligned}$$

$$\omega_c = \frac{1}{RC}$$

$$|H| = \frac{1}{\sqrt{1 + \frac{\omega_c^2}{\omega^2}}} \quad \angle H = + \tan^{-1} \frac{\omega_c}{\omega}$$

FOR BOTH FILTERS

$$|H| = \frac{1}{\sqrt{1 + \frac{\omega_c^2}{\omega^2}}} = \frac{1}{\sqrt{2}} \quad \omega = \omega_c$$


$$\approx .707 \quad \omega = .1 \omega_c$$

$$\approx 1 \quad \omega = 10 \omega_c$$


$$\angle H = \tan^{-1} \frac{\omega_c}{\omega} = +45^\circ \quad \omega = \omega_c$$

$$\approx +90^\circ \quad \omega \rightarrow 0 \quad \frac{\omega_c}{\omega} \rightarrow \infty$$
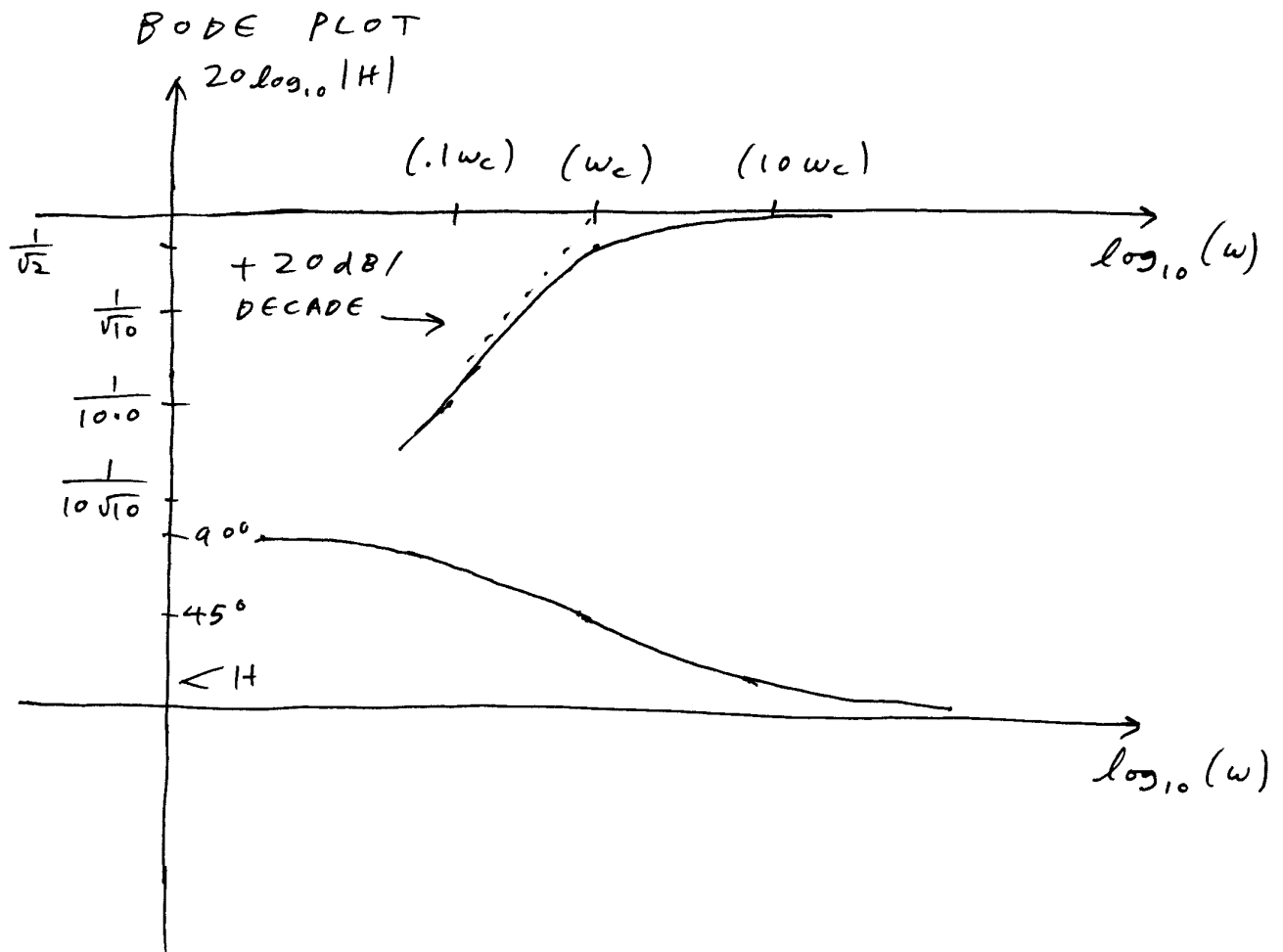
$$\approx 0^\circ \quad \omega \rightarrow \infty \quad \frac{\omega_c}{\omega} \rightarrow 0$$




COMBINE FILTERS

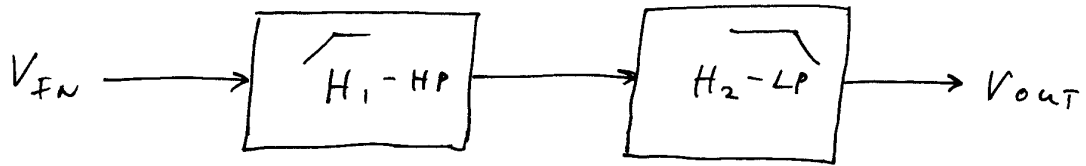

$$H = H_1(\omega) \cdot H_2(\omega)$$
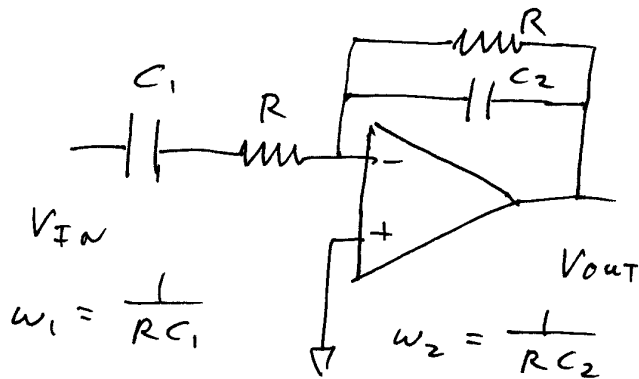
$$\log_{10} H = \log_{10} H_1 + \log_{10} H_2$$




$$\omega_1 < \omega_2$$

$$H = \left(\frac{1}{1 + \frac{\omega_1}{j\omega}} \right) \left(\frac{1}{1 + j\frac{\omega}{\omega_2}} \right)$$

$$|H| = \frac{1}{\sqrt{1 + \frac{\omega_1^2}{\omega^2}} \sqrt{1 + \frac{\omega^2}{\omega_2^2}}}$$

$$\angle H = \tan^{-1} \frac{\omega_1}{\omega} + \tan^{-1} \frac{\omega}{\omega_2}$$

DOES THIS WORK?

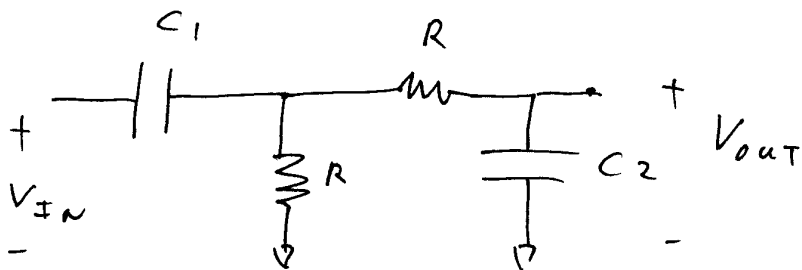

COMBINED FILTER $\omega_2 \approx 10 \omega_1$

$$|H| = \frac{1}{\sqrt{1 + \frac{\omega_1^2}{\omega^2}}} \frac{1}{\sqrt{1 + \frac{\omega^2}{\omega_2^2}}}$$

$$\angle H = \tan^{-1} \frac{\omega_1}{\omega} - \tan^{-1} \frac{\omega}{\omega_2}$$

ω	$ H $	$\angle H$
$.1 \omega_1$	$(.1)(1)$	$+90^\circ$
ω_1	$(\frac{1}{\sqrt{2}})(1)$	45°
ω_2	$(1)(\frac{1}{\sqrt{2}})$	-45°
$10 \omega_2$	$(1)(.1)$	-90°

BODE PLOT

