

AC POWER

$$p(t) = v(t) \cdot i(t)$$

ALWAYS!

AVG POWER


$$P = \frac{1}{T} \int_0^T p(t) dt$$

$$= \frac{1}{T} \int_0^T v(t) i(t) dt$$

FOR $v(t) = \cos \omega t$,

$\omega T = 2\pi$ (ONE CYCLE)

$$T = \frac{2\pi}{\omega}$$

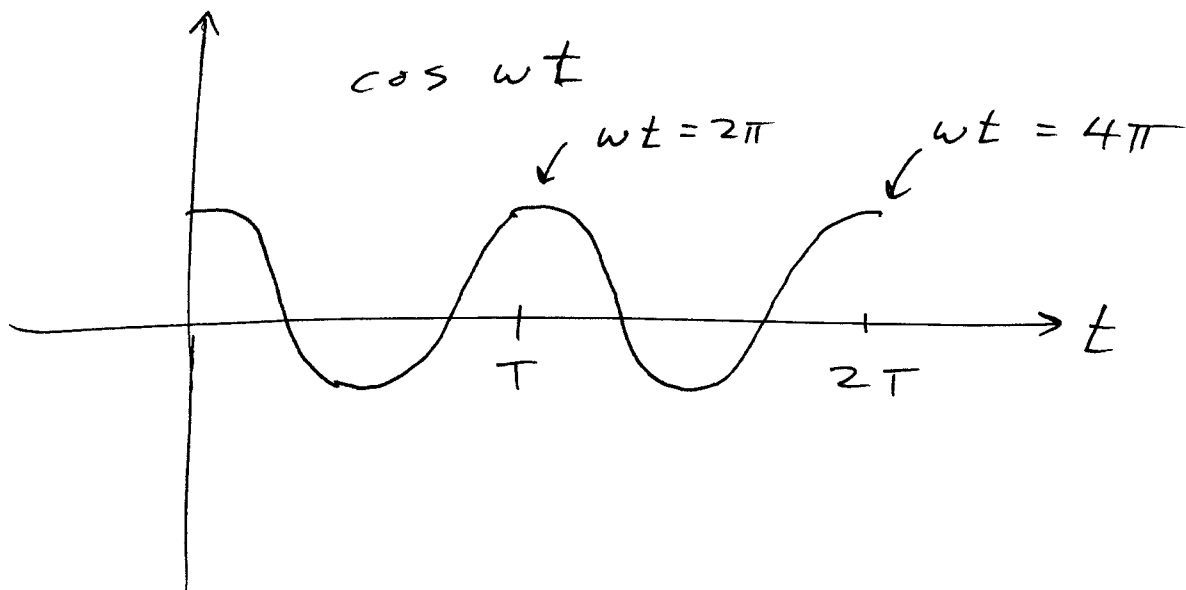

RESISTOR

$$v(t) = R i(t)$$

$$p(t) = v(t) i(t) = R i^2(t)$$

$$\text{AVG POWER } P = \frac{1}{T} \int_0^T R i^2(t) dt$$


$$\text{FOR } i(t) = I_p \cos \omega t$$

$$i^2(t) = I_p^2 \cos^2 \omega t \quad \text{AVG } 0$$

$$= I_p^2 \left(\frac{1}{2} + \frac{1}{2} \cos 2\omega t \right)$$

AVG $\frac{1}{2}$

$$P = \frac{1}{2} R I_p^2$$

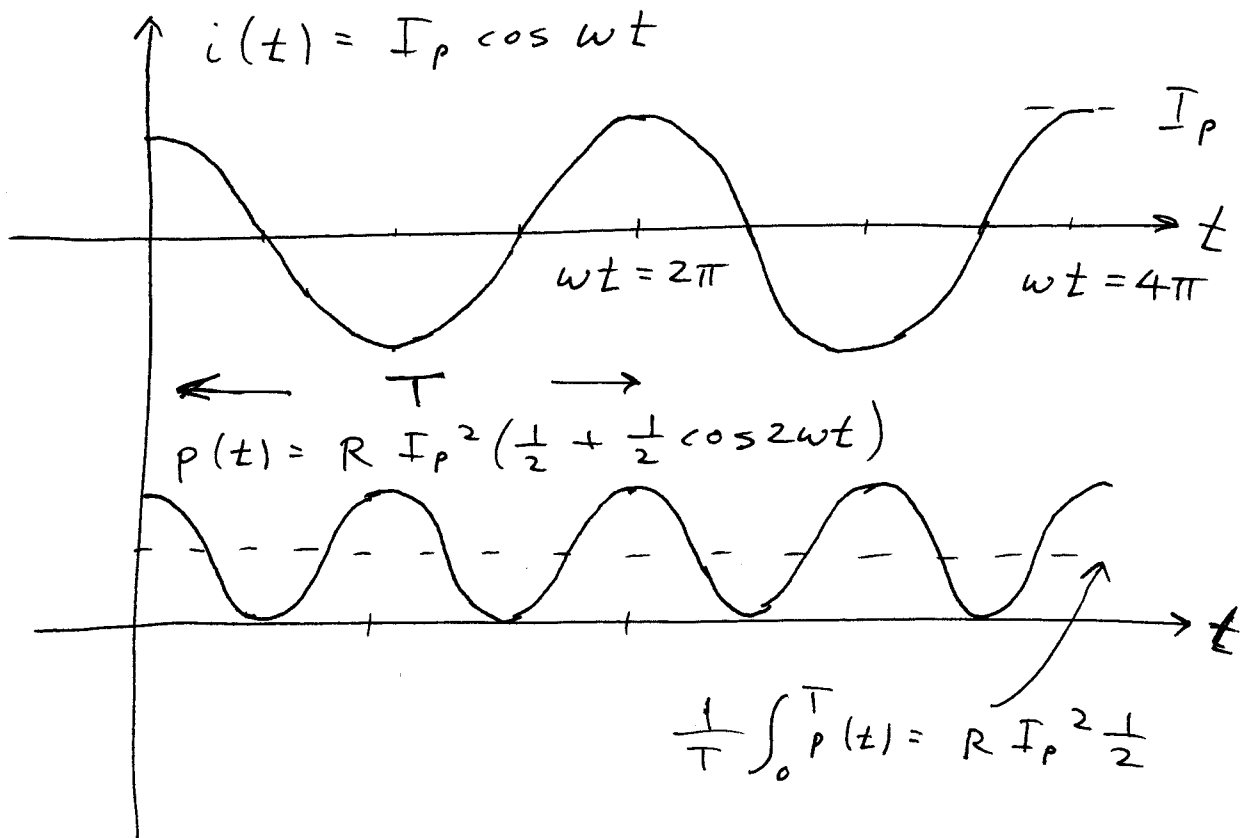

THIS RMS BUSINESS

$$p(t) = R i^2(t)$$

$$\text{AVG} \{ p(t) \} = \text{AVG} \{ R i^2(t) \}$$

$$= R \text{AVG} \{ i^2(t) \}$$

R JUST
SCALES
EVERYTHING

$$= R \left(\sqrt{\text{AVG} \{ i^2(t) \}} \right)^2$$

$$= R I_{\text{RMS}}^2$$

$$\text{WHERE "I}_{\text{EFF}}" = I_{\text{RMS}} = \sqrt{\text{AVG} \{ i^2(t) \}}$$

$$\text{FOR } i(t) = I_p \cos \omega t$$

$$\text{AVG} \{ i^2(t) \} = \frac{1}{2} I_p^2$$

$$I_{\text{RMS}} = \sqrt{\frac{1}{2} I_p^2}$$

$$= \frac{1}{\sqrt{2}} I_p !$$

$$\text{WALL OUTLET: } V_{\text{RMS}} = 120 \text{ V}$$

$$v(t) = \sqrt{2} (120) \cos \left(\frac{2\pi}{T} t \right)$$

$$\hookrightarrow \omega = \frac{2\pi}{T}$$

$$\frac{1}{T} = 60 \text{ Hz}$$

$$v(t) = 170 \cos(377 t)$$

$$\hookrightarrow 2\pi(60 \text{ Hz})$$

$$377 \text{ RAD/S}$$

APPARENT POWER

$$|S| = |V_{RMS}| |I_{RMS}| = \left| \frac{V}{\sqrt{2}} \right| \left| \frac{I}{\sqrt{2}} \right|$$

↑
REASON FOR
NOTATION GIVEN
LATER

POWER FACTOR

$$P.F. = \frac{\text{AVG POWER}}{\text{APPARENT POWER}}$$

$$\text{RESISTOR P.F.} = \frac{R |I_{RMS}|^2}{R |I_{RMS}| |I_{RMS}|} = 1$$

INDUCTOR

$$v(t) = L \frac{di}{dt} \quad i(t) = \underbrace{\sqrt{2} I_{RMS}}_{I_p} \cos \omega t$$

$$v(t) = \omega L \sqrt{2} I_{RMS} (-\sin \omega t)$$

$$p(t) = v \cdot i = 2 \omega L I_{RMS}^2 \cos \omega t (-\sin \omega t)$$

$$= 2 \omega L I_{RMS}^2 \frac{1}{2} (-\sin 2\omega t)$$

$$= -Q \sin 2\omega t$$

$$Q = \omega L I_{RMS}^2$$

INDUCTOR POWER

$$P = \text{AVG}(-Q \sin 2\omega t) = 0!$$

AVG POWER

$$Q = \omega L I_{\text{RMS}}^2$$

REACTIVE POWER

$$\text{P.F.} = \frac{P}{|V_{\text{RMS}}| |I_{\text{RMS}}|} = ?$$

$$|S| = |V_{\text{RMS}}| |I_{\text{RMS}}| = \left| \frac{j\omega L I}{\sqrt{2}} \right| \left| \frac{I}{\sqrt{2}} \right|$$

APPARENT POWER $= \frac{\omega L}{2} I_p^2 = \omega L I_{\text{RMS}}^2 = Q!$

$$\text{P.F.} = \frac{P}{|S|} = \frac{0}{Q} = 0$$

CAPACITOR

$$v(t) = \frac{1}{C} \int i(t) dt \quad i(t) = \sqrt{2} I_{\text{RMS}} \cos \omega t$$

$$v(t) = \frac{\sqrt{2}}{\omega C} I_{\text{RMS}} \sin \omega t$$

$$p(t) = v \cdot i = \frac{(\sqrt{2})(\sqrt{2})}{\omega C} I_{\text{RMS}} I_{\text{RMS}} \cos \omega t \sin \omega t$$

$$= \frac{2}{\omega C} I_{\text{RMS}}^2 \frac{1}{2} \sin 2\omega t$$

$$= -Q \sin 2\omega t$$

$$Q = - \frac{I_{\text{RMS}}^2}{\omega C}$$

CAPACITOR POWER

$$P = \text{AVG}(-Q \sin 2\omega t) = 0$$

$$Q = -\frac{I_{\text{RMS}}^2}{\omega C}$$

$$|S| = \frac{1}{\omega C} |I_{\text{RMS}}|^2 = |Q|$$

$$\text{P.F.} = \frac{P}{|S|} = 0!$$

MEANING OF Q - REACTIVE POWER

$$\text{RESISTOR } P = |S| = |V_{\text{RMS}}| |I_{\text{RMS}}|$$

GIVEN \nearrow
VOLTAGE, CURRENT
DELIVERING AVG POWER

$$\text{CAPACITOR } P = 0 \leftarrow \text{NO AVG POWER}$$

INDUCTOR

$$|S| = |Q| = |V_{\text{RMS}}| |I_{\text{RMS}}|$$

\nearrow
DRAWING
CURRENT

$$Q > 0$$

(INDUCTOR - CURRENT
LAGS VOLTAGE)

$$Q < 0$$

(CAPACITOR - CURRENT
LEADS VOLTAGE)


RMS PHASOR $v(t) = V_p \cos \omega t + \phi_V$

$$V_{\text{RMS}} = \frac{1}{\sqrt{2}} V \quad |V_{\text{RMS}}| = \frac{1}{\sqrt{2}} V_p$$

PHASOR PHASOR

USE RMS PHASOR IN POWER PROBLEMS UNLESS OTHERWISE STATED

REACTIVE POWER ADDS (SERIES OR PARALLEL)

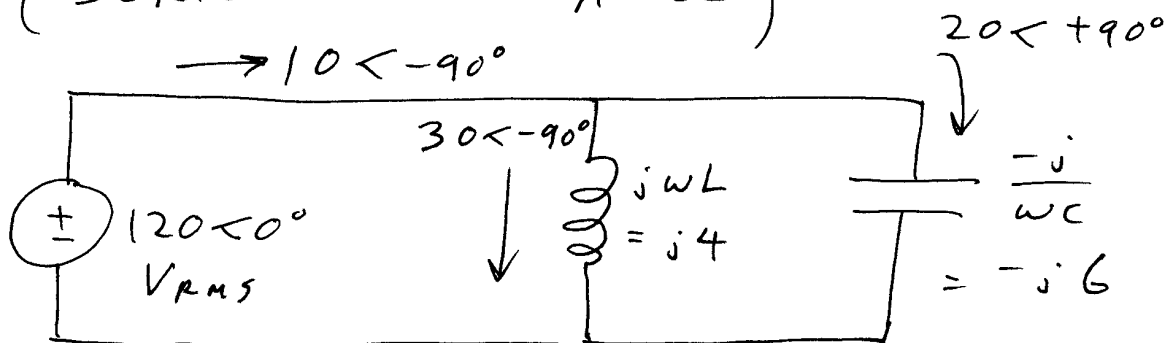

$$Q_L = \omega L (30^2) = 4(900) = 3600 \quad Q_{\text{EFF}} = 1200$$

$$Q_C = -\frac{(20)^2}{\omega C} = -6(400) = -2400$$

