

ADDING 2-BITS (HALF ADDER)

a_0	b_0	S_0	C_0
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


SUM

$$S_0 = a_0 \oplus b_0$$

(EXCLUSIVE OR -
 a_0 OR b_0 BUT NOT
 BOTH)

$$C_0 = a_0 \cdot b_0$$

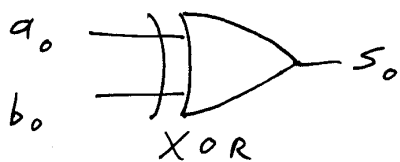(AND: BOTH $a_0 = 1$
 AND $b_0 = 1$ FOR $C_0 = 1$)



BUILDING - BLOCK LOGIC FUNCTIONS

AND

a	b	c
0	0	0
0	1	0
1	0	0
1	1	1

$c = a \cdot b$
 LOGICAL PRODUCT

OR

a	b	c
0	0	0
0	1	1
1	0	1
1	1	1

$c = a + b$
 LOGICAL SUM

TRUTH TABLE

NOT

a	\bar{a}
0	1
1	0

$\bar{a} = \text{NOT}(a)$
 LOGICAL COMPLEMENT

REDUCING "XOR" TO THE BUILDING BLOCKS

a_0	b_0	F	g	S_0
0	0	0	0	0
0	1	1	0	1
1	0	0	1	1
1	1	0	0	0

$$S_0 = F + g$$

\bar{a}_0	b_0	$F = \bar{a}_0 \cdot b_0$	a_0	\bar{b}_0	$g = a_0 \cdot \bar{b}_0$
1	0	0	0	1	0
1	1	1	0	0	0
0	0	0	1	1	1
0	1	0	1	0	0

SUM-OF-PRODUCTS REALIZATION

$$S_0 = F + g = \bar{a}_0 \cdot b_0 + a_0 \bar{b}_0$$

FROM TRUTH TABLE


	a_0	b_0	$\bar{a}_0 \cdot \bar{b}_0$	$\bar{a}_0 \cdot b_0$	$a_0 \cdot \bar{b}_0$	$a_0 \cdot b_0$	S_0
$\bar{a}_0 \bar{b}_0$	0	0	1	0	0	0	0
$\bar{a}_0 b_0$	0	1	0	1	0	0	1
$a_0 \bar{b}_0$	1	0	0	0	1	0	1
$a_0 b_0$	1	1	0	0	0	1	0



"MIN TERMS"

2-LEVEL SUM OF PRODUCTS
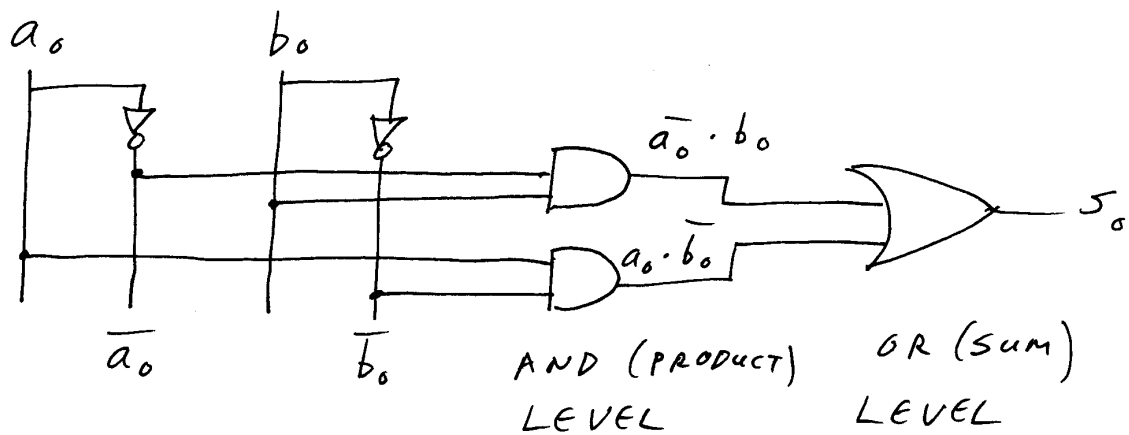
$$S_0 = \bar{a}_0 \cdot b_0 + a_0 \bar{b}_0$$



INSTEAD OF FOCUSING ON "1"s,
LOOK AT "0"s

a_0	b_0	$S_0 = P \cdot Q$		
0	0	0	0	1 $\leftarrow P$ SUPPLIES 0 HERE
0	1	1	1	1
1	0	1	1	1
1	1	0	1	0 $\leftarrow Q$ SUPPLIES 0 HERE


MAX TERMS

	$a_0 + b_0$	$a_0 + \bar{b}_0$	$\bar{a}_0 + b_0$	$\bar{a}_0 + \bar{b}_0$	
$a_0 + b_0$	0	1	1	1	✓
$a_0 + \bar{b}_0$	1	0	1	1	
$\bar{a}_0 + b_0$	1	1	0	1	
$\bar{a}_0 + \bar{b}_0$	1	1	1	0	✓

$$S_0 = (a_0 + b_0) \cdot (\bar{a}_0 + \bar{b}_0)$$

2-LEVEL PRODUCT OF SUMS
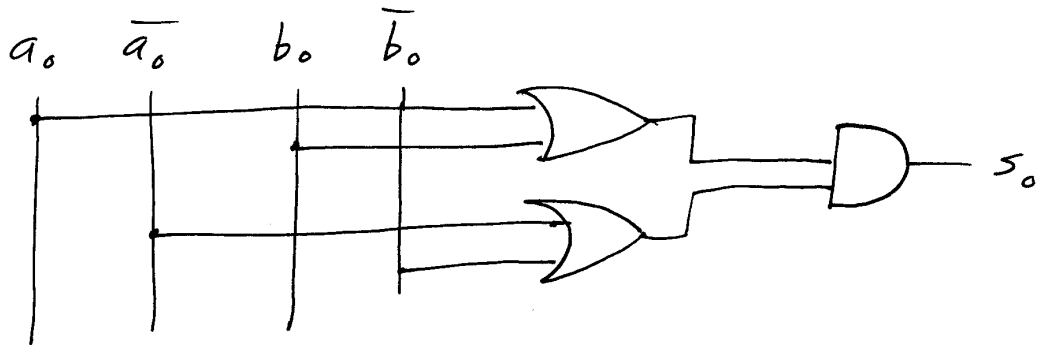
$$S_0 = (a_0 + b_0) \cdot (\bar{a}_0 + \bar{b}_0)$$



(INVERTERS NOT SHOWN)

DE MORGAN'S THEOREM

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

$$\overline{A + B} = \bar{A} \cdot \bar{B}$$

PROOF





A	B	\bar{A}	\bar{B}	$A \cdot B$	$\overline{A \cdot B}$	$A + B$	$\overline{A + B}$	$\bar{A} \cdot \bar{B}$	$\bar{A} + \bar{B}$
0	0	1	1	0	1	0	1	1	1
0	1	1	0	0	1	1	0	0	1
1	0	0	1	0	1	1	0	0	1
1	1	0	0	1	0	1	0	0	0

MY FIRST JOB IN ACCOUNTING
DATA PROCESSING


IF (AGE < 60) AND (PAY < 2000)
 INVITE_TO_PICNIC ← ELIMINATE
ELSE
 LAY OFF PICNIC

IF (AGE ≥ 60) OR (PAY ≥ 2000)
 LAY OFF

APPLICATION TO LOGIC CIRCUITS

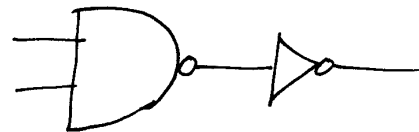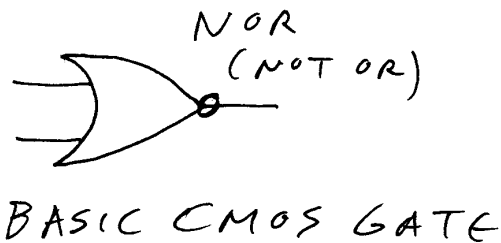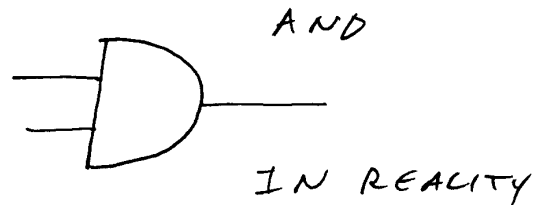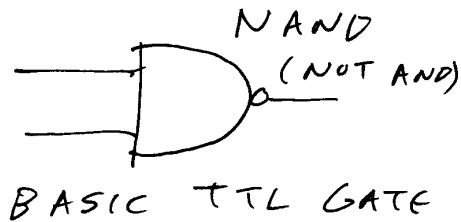


BOTH NAND

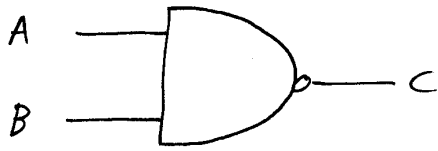


$$C = \overline{A \cdot B}$$

DE MORGAN

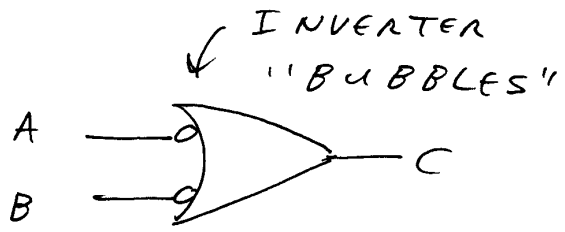


$$C = \overline{\overline{A} + \overline{B}}$$

BOTH NOR

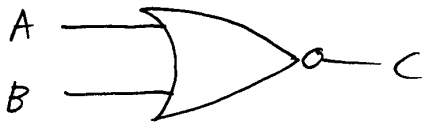

$$C = \overline{A + B}$$

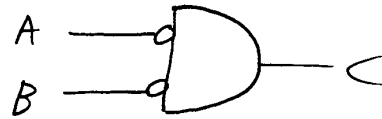


$$C = \overline{\overline{A} \cdot \overline{B}}$$

2-LEVEL SUM OF PRODUCTS

$$S_0 = \overline{a_0} b_0 + a_0 \overline{b_0}$$

a_0 b_0

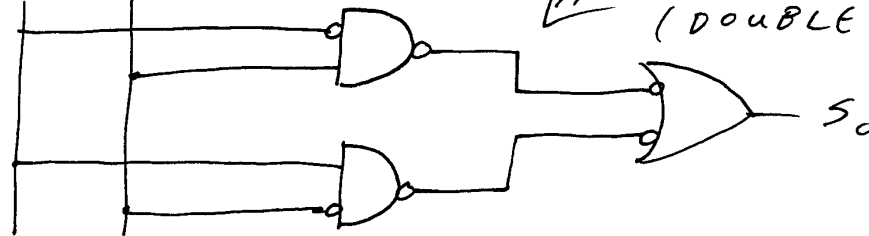

INVERTER BUBBLES


1-INPUT NAND



SAME AS





TIE INPUTS

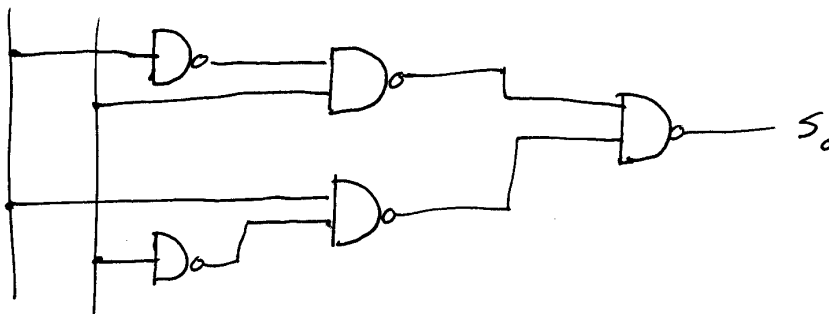

2-LEVEL PRODUCT OF SUMS
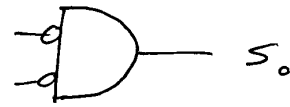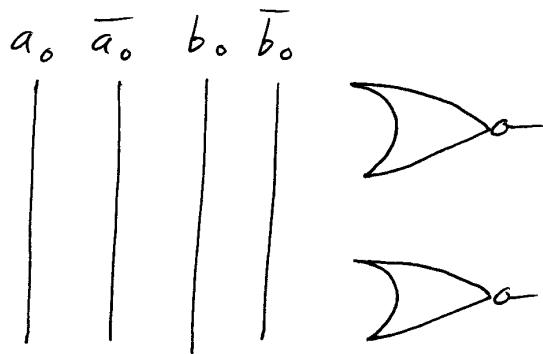
$$S_0 = (a_0 + b_0)(\bar{a}_0 + \bar{b}_0)$$



↑
WHAT KIND
OF GATE?

FULL ADDER

c_0	a_1	b_1	s_1	c_1
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

SOP $s_1 =$

POS $c_1 =$