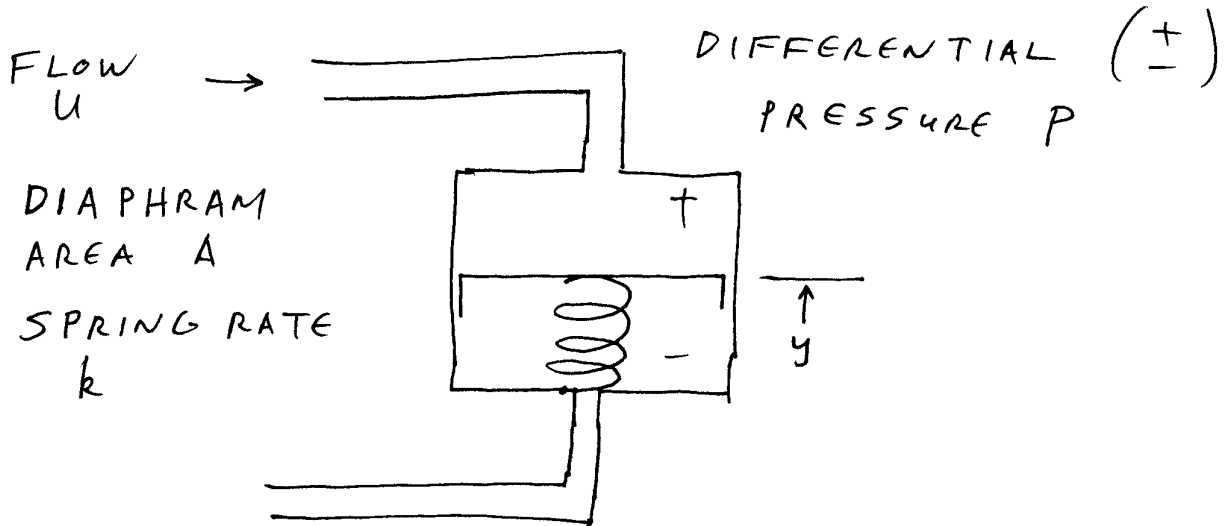


# INDUCTOR (L) AND CAPACITOR (C)

## 2-PORT HYDRAULIC ACCUMULATOR



$$F = ky \quad P = \frac{F}{A}$$

$$y = \frac{\Delta V_{OL}}{A} \quad \Delta V_{OL} = \int U dt$$


SO

$$P = \frac{k}{A^2} \int U dt$$

$$U = \frac{A^2}{k} \frac{dP}{dt} = C \frac{dP}{dt}$$

FOR  $C = \frac{A^2}{k}$  BIG  $A$ , SOFT SPRING, BIG  $C$

## 2-PORT ELECTRIC ACCUMULATOR

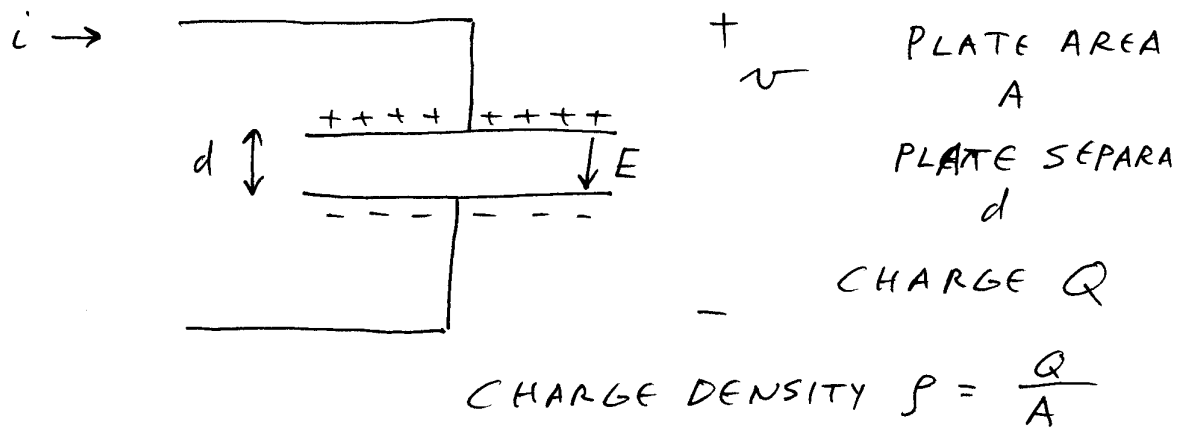

$$E = \frac{1}{\epsilon} \rho \quad v = Ed$$

$$\text{SO} \quad v = Ed = \frac{1}{\epsilon} \frac{Q}{A} d$$

$$Q = \int i dt$$


$$v = \frac{1}{C} \int i dt$$

$$i = C \frac{dv}{dt}$$

$$C = \frac{\epsilon A}{d}$$

FOR BIG  $C$ , NEED BIG  $\epsilon$ ,  $A$   
SMALL  $d$

# HYDRAULIC INERTIA

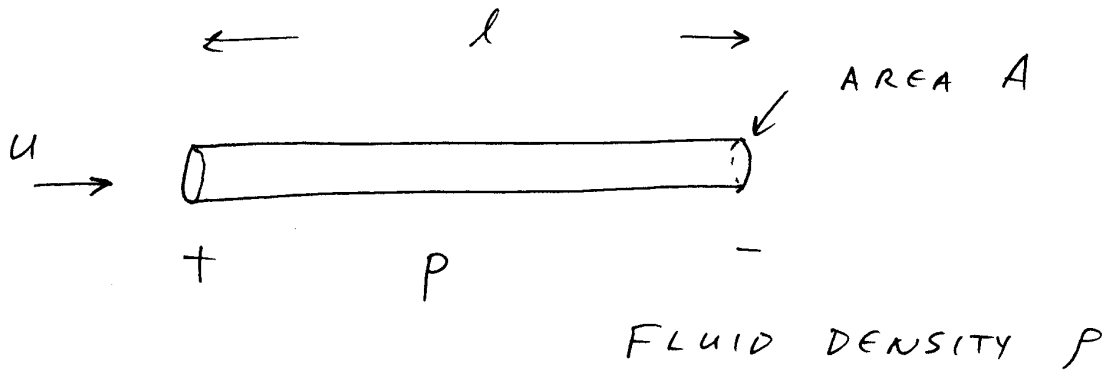

$$F = m \frac{dv}{dt}$$

$$v = \frac{u}{A}$$

$$m = \rho l A$$

$$P = \frac{F}{A}$$

SO  $F = m \frac{dv}{dt}$

$$P = \frac{m}{A} \frac{dv}{dt}$$

$$P = \rho l \frac{d}{dt} \frac{u}{A}$$

$$= \frac{\rho l}{A} \frac{d}{dt} u$$


$$P = L \frac{d}{dt} u$$

$$u = \frac{1}{L} \int P dt$$

BIG L NEEDS  
BIG  $\rho$ , LONG  
TUBE, NARROW  
TUBE

$$L = \frac{\rho l}{A}$$

## MAGNETIC INERTIA

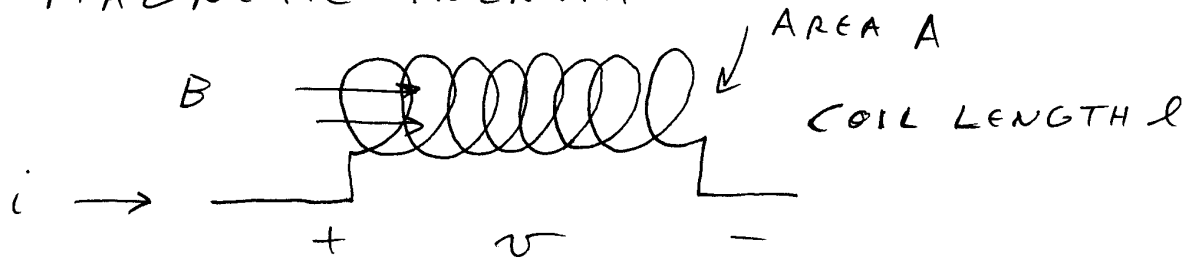

$B$  : MAGNETIC FIELD

$\phi = B \cdot A$  MAGNETIC FLUX

$\phi = N \cdot i \cdot \mu \frac{A}{l}$   $N$  : TURNS OF WIRE

$\mu$  MAGNETIC PERMEABILITY

## FARADAY LAW OF MAGNETIC INDUCTION

$$\mathcal{V} = N \frac{d\phi}{dt}$$

$$= N^2 \mu \frac{A}{l} \frac{di}{dt}$$

$$\mathcal{V} = L \frac{di}{dt} \quad L = N^2 \mu \frac{A}{l}$$

BIG  $L$  MANY TURNS  $N$   
HIGH  $\mu$  (IRON)  
LARGE, SQUAT COIL

ALSO  $i = \frac{1}{L} \int \mathcal{V} dt$

## INDUCTOR

$$v = L \frac{di}{dt} \quad i = \frac{1}{L} \int v dt$$

INDUCTANCE

L UNIT H (HENRY)

## CAPACITOR

$$i = C \frac{dv}{dt} \quad v = \frac{1}{C} \int i dt$$

CAPACITANCE


C UNIT F (FARAD)

## SINUSOIDAL SIGNALS

$$v_1(t) = \cos \omega t$$

$$v_2(t) = \sin \omega t = \cos \omega t - 90^\circ$$
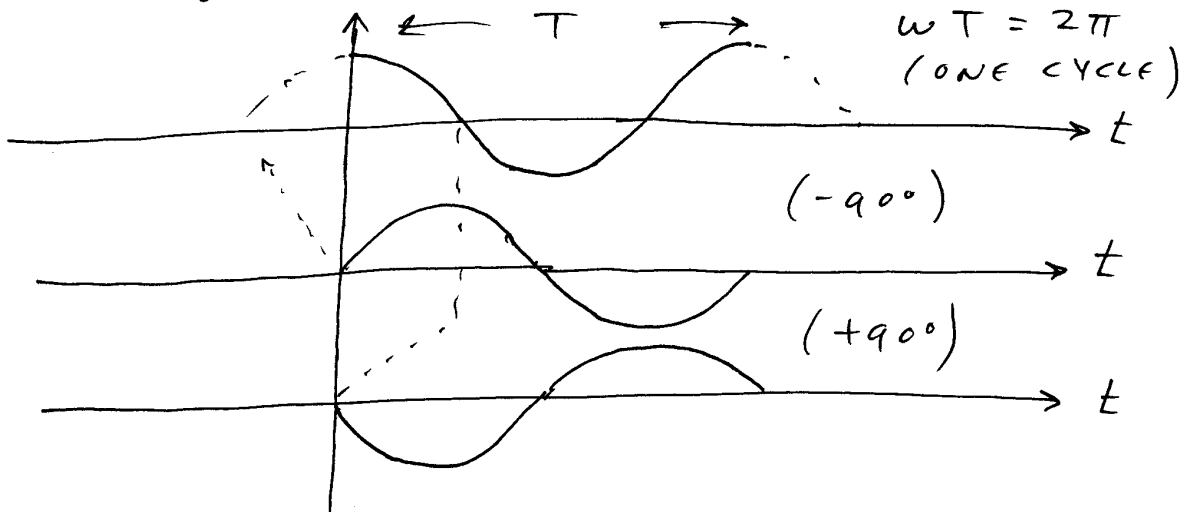
$$v_3(t) = -\sin \omega t = \cos \omega t + 90^\circ$$



$$v(t) = \cos \omega t$$

$$\frac{dv(t)}{dt} = -\omega \sin \omega t = \omega \cos \omega t + 90^\circ$$


$$\int v(t) dt = \frac{1}{\omega} \sin \omega t = \frac{1}{\omega} \cos \omega t - 90^\circ$$

$$i(t) = \sin \omega t = \cos \omega t - 90^\circ$$

$$\frac{di(t)}{dt} = \omega \cos \omega t \begin{matrix} \swarrow +90^\circ \\ \downarrow -90^\circ \end{matrix}$$

$$\int i(t) dt = -\frac{1}{\omega} \cos \omega t = \frac{1}{\omega} \cos \omega t - 180^\circ$$

INDUCTORS IN SERIES

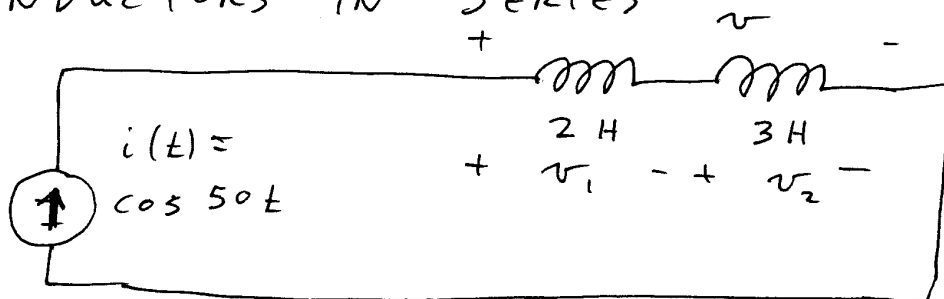

$$v_1 = L_1 \frac{di}{dt} = (2) \frac{d}{dt} \cos 50t$$

$$= -100 \sin 50t$$


$$v_2 = L_2 \frac{di}{dt} = (3) \frac{d}{dt} \cos 50t$$

$$= -150 \sin 50t$$

$$v_3 = -250 \sin 50t = (5) \frac{d}{dt} \cos 50t$$

$$= 5 \frac{di}{dt}$$

## INDUCTORS IN PARALLEL

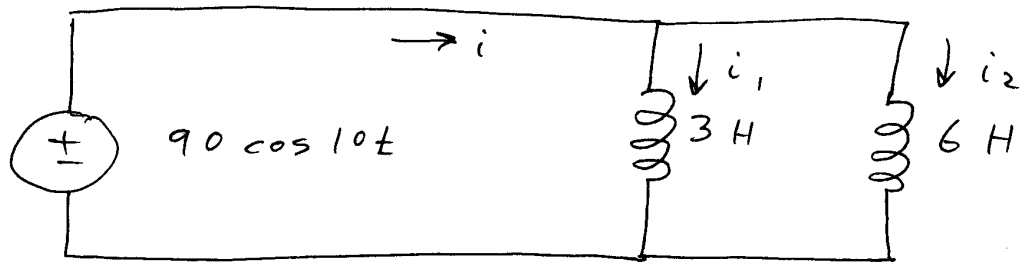

$$i_1 = \frac{1}{L_1} \int v dt = \frac{1}{3} \int 90 \cos 10t dt$$

$$= \frac{90}{(3)(10)} \sin 10t = 3 \sin 10t$$

$$i_2 = \frac{1}{L_2} \int v(t) dt = \frac{1}{6} \int 90 \cos 10t dt$$

$$= \frac{90}{(6)(10)} \sin 10t = 1.5 \sin 10t$$


$$i(t) = i_1 + i_2 = \left( \frac{1}{3} + \frac{1}{6} \right) \frac{90}{10} \sin 10t$$

$$= \left( \frac{1}{3} + \frac{1}{6} \right) \int 90 \cos 10t dt$$


$$= \frac{1}{L_{\text{EFF}}} \int v dt$$

$$L_{\text{EFF}} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2}} = L_1 \parallel L_2$$


## CAPACITORS IN //

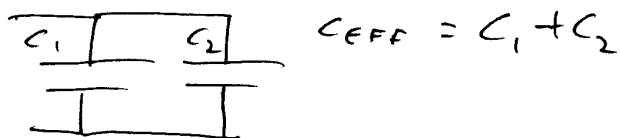

## IN SERIES

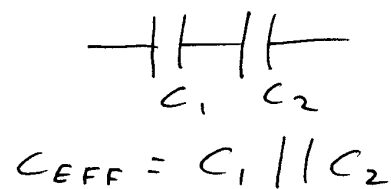


## CAPACITORS IN SERIES

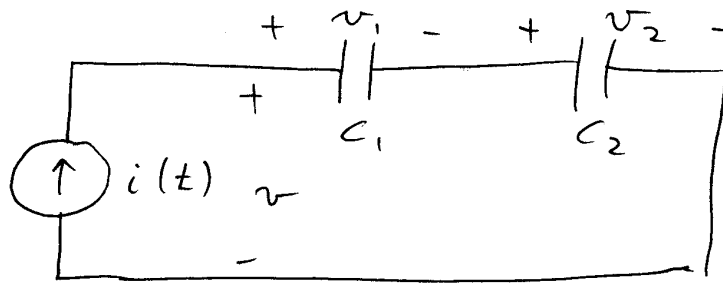

$$v_1 = \frac{1}{C_1} \int i dt \quad v_2 = \frac{1}{C_2} \int i dt$$

$$\begin{aligned} v &= \left( \frac{1}{C_1} + \frac{1}{C_2} \right) \int i dt \\ &= \frac{1}{C_{EFF}} \int i dt \end{aligned}$$

## CAPACITORS IN PARALLEL

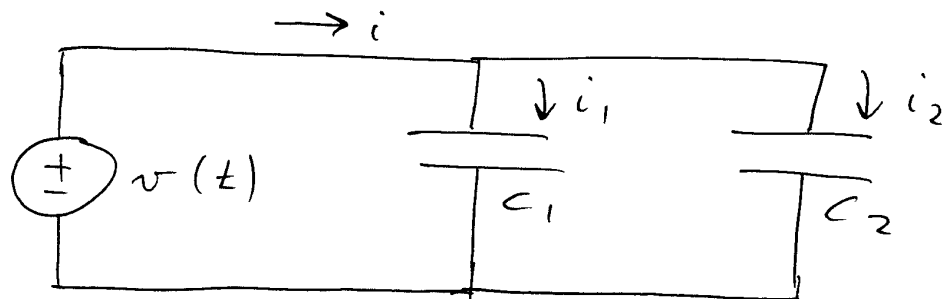

$$i_1 = C_1 \frac{dv}{dt} \quad i_2 = C_2 \frac{dv}{dt}$$

$$\begin{aligned} i &= i_1 + i_2 = (C_1 + C_2) \frac{dv}{dt} \\ &= C_{EFF} \frac{dv}{dt} \end{aligned}$$